

Introduction to neural networks – Assignment 1 – RC circuits

By: Nadav Porat , ID: 207825506

In this page I will write the final answers, in the next pages the calculations and code are added.

Question 1

The voltage on each pair of capacitor is the same because they all carry a total of $6\mu F$:

$$V_1 = V_2 = V_3 = 4[v]$$

The charge:

$$Q_1 = 4\mu F, Q_2 = 20\mu F, Q_3 = 8\mu F, Q_4 = 16\mu F, Q_5 = Q_6 = 12\mu F$$

Question 2

a. While charging:

$$I_c = \frac{dq}{dt} = \frac{\epsilon}{R} e^{-\frac{t}{RC}}, V = \frac{q}{c} = \epsilon(1 - e^{-\frac{t}{RC}})$$


b. From the graph:

$$V_0 = \epsilon \cong 11.94[v], R \cong 3[k\Omega]$$


$$I(0) \cong 4[milA], I(20) \cong 1.05[milA]$$

Question 3

a.

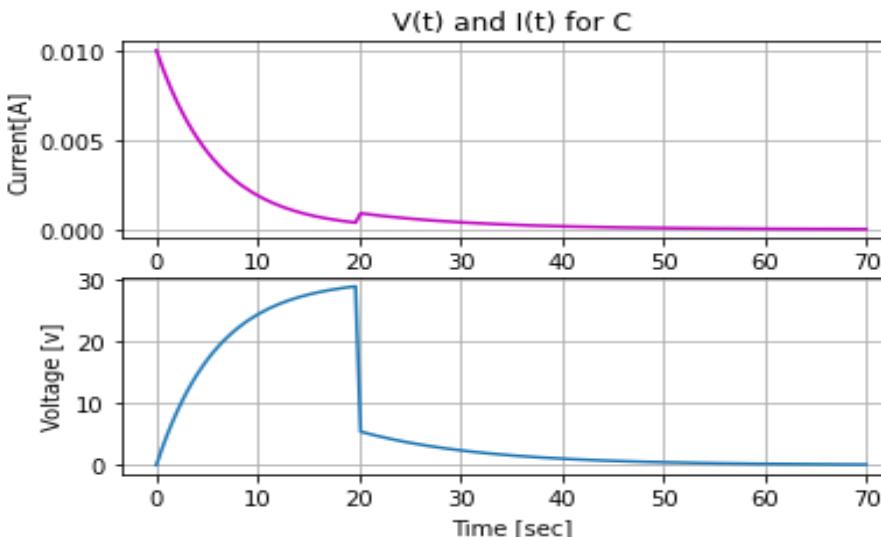


$$c_{eq} = C + C = 2C$$

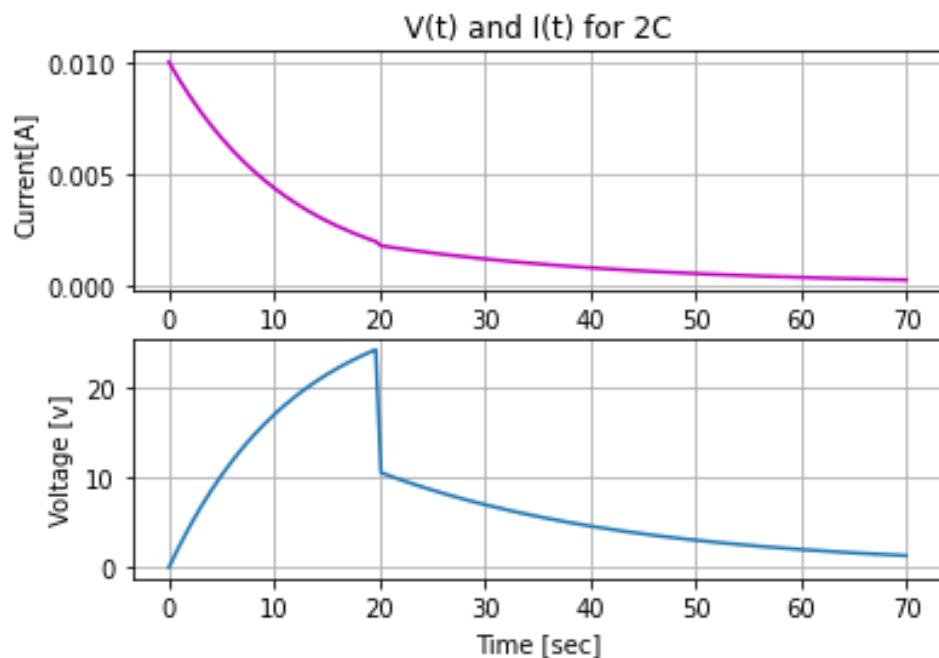

b2.

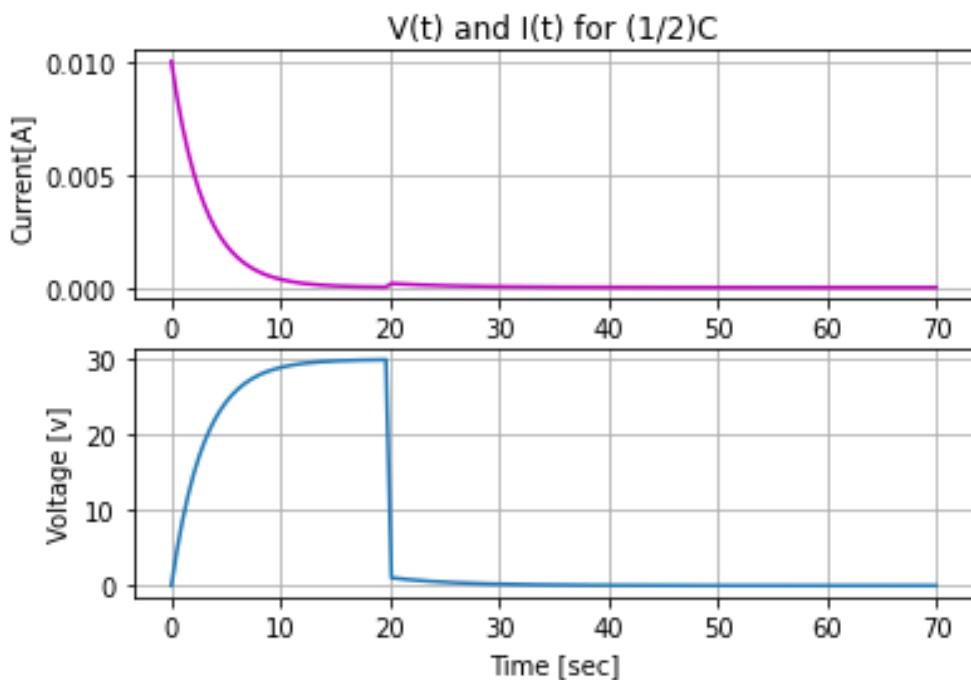
$$c_{eq} = \left(\frac{1}{C} + \frac{1}{C} \right)^{-1} = \frac{C}{2}$$



רוכסן : SCN
207825506 : ס.ד.

1. סדרת סכמתן מודולית

1 > 8KO

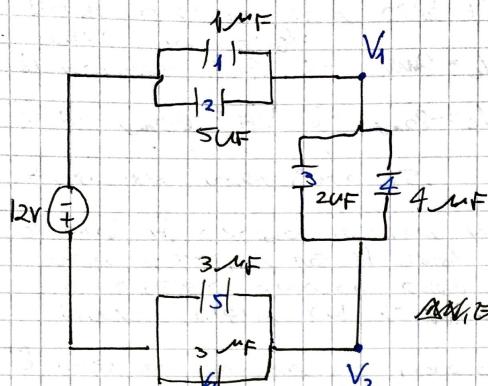

פ'3) מודול של סכמתן סדרת סכמתן מודולית
אילך בפ' 2 מגדיר מודול סדרת סכמתן מודולית


$$\alpha_1 = C_1 \Delta V_1, \alpha_2 = C_2 \Delta V_1$$

$$\alpha_3 = C_3 \Delta V_2, \alpha_4 = C_4 \Delta V_2$$

$$\alpha_5 = C_5 \Delta V_3, \alpha_6 = C_6 \Delta V_3$$

האנו

: מודול סדרת סכמתן מודולית

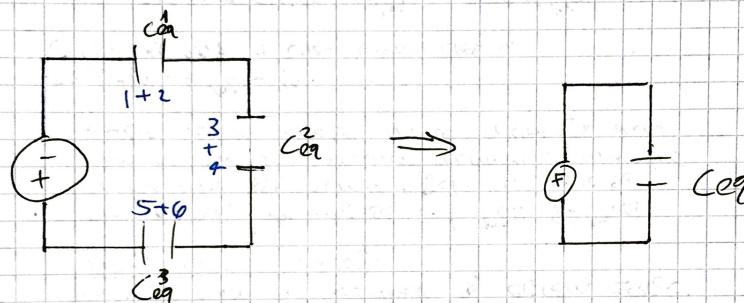

$$\frac{1}{C_{eq}} = \frac{1}{C_{eq}^{(1)}} + \frac{1}{C_{eq}^{(2)}} + \frac{1}{C_{eq}^{(3)}} \Rightarrow C_{eq} = \left(\sum \frac{1}{C_{eq}(i)} \right)^{-1}$$

$$C_{eq}^{(1)} = C_1 + C_2, \quad C_{eq}^{(2)} = C_3 + C_4, \quad C_{eq}^{(3)} = C_5 + C_6$$

הנ"ל מוגדר מודול סדרת סכמתן מודולית כה שפ' 2 מגדיר מודול סדרת סכמתן מודולית. מודול סדרת סכמתן מודולית מוגדר כה שפ' 2 מגדיר מודול סדרת סכמתן מודולית.

$$Q_{eq} = Q_{eq}^{(1)} = Q_{eq}^{(2)} = Q_{eq}^{(3)}$$

: מודול סדרת סכמתן מודולית

$$Q_{eq} = C_{eq} V_{tot} = 12 C_{eq}$$

$$C_{eq}^{(1)} = C_{eq}^{(2)} = C_{eq}^{(3)} = 6\mu F \Rightarrow C_{eq} = \frac{6}{3} \mu F$$




$$\Rightarrow Q_{eq} = Q_{eq}^{(1)} = Q_{eq}^{(2)} = Q_{eq}^{(3)} = 12 C_{eq} = 24 \mu C$$

~~$$\Rightarrow Q_{eq} = Q_{eq}^{(1)} = Q_{eq}^{(2)} = Q_{eq}^{(3)}$$~~

$$\Rightarrow V_1 = V_2 = V_3 = \frac{Q_{eq}^{(1)}}{C_{eq}^{(1)}} = \frac{24 \mu C}{6 \mu F} = 4 V$$

$$\Rightarrow \alpha_1 = 4 \mu C, \alpha_2 = 20 \mu C, \alpha_3 = 8 \mu C, \alpha_4 = 16 \mu C$$

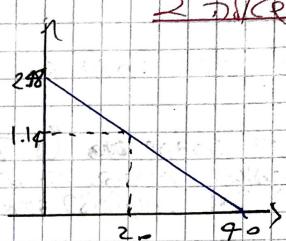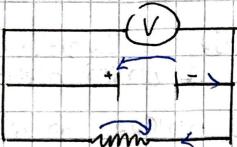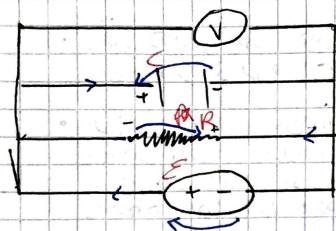~~$$\alpha_5 = 12 \mu C, \alpha_6 = 12 \mu C$$~~



$$Q(t) = \Sigma C \left(1 - e^{-\frac{t}{RC}}\right) \Rightarrow I_c = \frac{dQ}{dt} = \frac{\Sigma C}{R} e^{-\frac{t}{RC}}$$

$$Q = Vc \Rightarrow V = \frac{Q}{C} \quad \text{and} \quad V(t) = \Sigma \left(1 - e^{-\frac{t}{RC}}\right)$$

(6) : 11.94V

$$\text{KVL} \rightarrow \text{Voltage drop across } RC \text{ circuit is } 2.48 \text{ V at } t=0$$

$$V_c = Q/C \Rightarrow I = C \frac{dV}{dt}, \quad V_c + V_R = V_c + IR = V_c + \frac{dV}{dt} \cdot R = 0$$

$$\Rightarrow \frac{dV_c}{dt} = -\frac{V_c}{RC} \Rightarrow V_c = V_0 e^{-\frac{t}{RC}}$$

$$\Rightarrow \ln(V_c(0)) = 2.48 \Rightarrow V_0 = \Sigma \approx 11.94V$$

(7) : R ~ 1kΩ

$$\text{Given } V_c(t) = \Sigma e^{-\frac{t}{RC}} \Rightarrow \ln\left(\frac{V}{\Sigma}\right) = -\frac{t}{RC}, \quad V_c(20) = \exp(1.14) = 3.13V$$

$$\Rightarrow R = \frac{t}{C} \left(\ln\left(\frac{\Sigma}{V}\right) \right)^{-1} \Rightarrow R = \frac{20s}{500\mu F} \left(\ln\left(\frac{11.94}{3.13}\right) \right)^{-1} \approx 3 \times 10^3 \Omega$$

+ 1kΩ


$R \approx 3k\Omega$

(8) : non-linear

$$I = \frac{V}{R} = \frac{\Sigma}{R} e^{-\frac{t}{RC}}$$

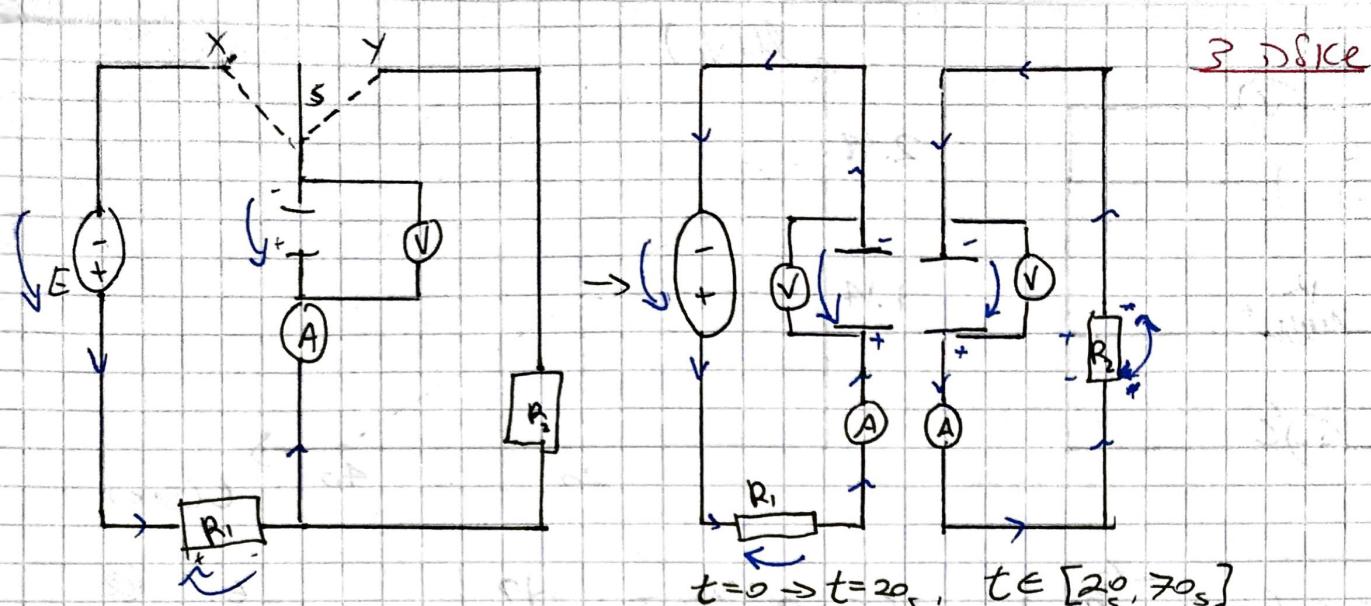(9) : non-linear

$$I(0) = \frac{\Sigma}{R} \approx 4[\text{mA}], \quad I(20) = \frac{\Sigma}{R} e^{-\frac{20}{RC}} \approx 1.05[\text{mA}]$$



$$V_E - V_R - V_C = 0 \Rightarrow E - \frac{dV_C}{dt} C R - V_C = 0$$


$$\Rightarrow \frac{dV_C}{dt} = -\frac{V_C}{RC} + \frac{E}{RC} \Rightarrow \frac{dV_C}{dt} + \frac{V_C}{RC} = \frac{E}{RC}$$

$$\Rightarrow V_C = V_0 e^{-\frac{t}{RC}}, V_0 = \text{const} = E$$


$$\Rightarrow V_C = E \left(1 - e^{-\frac{t}{RC}}\right), I_C = \frac{dQ}{dt} = \frac{d(V_C)}{dt} = \frac{E}{R_1} e^{-\frac{t}{RC}}$$

$$V_C^{\text{new}} + R_2 C \frac{dV}{dt} = 0 \Rightarrow V_C^{\text{new}} = V_0 e^{-\frac{t}{R_2 C}} \quad I_C = \frac{V_0}{R_2} e^{-\frac{t}{R_2 C}}$$

$$V_C(0) = V_0 = V_C^{\text{out}}(20)$$

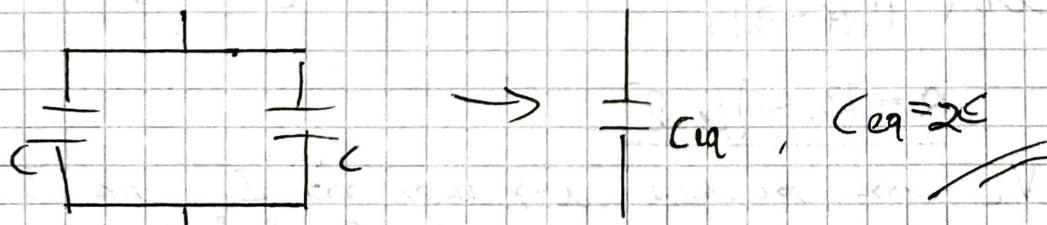
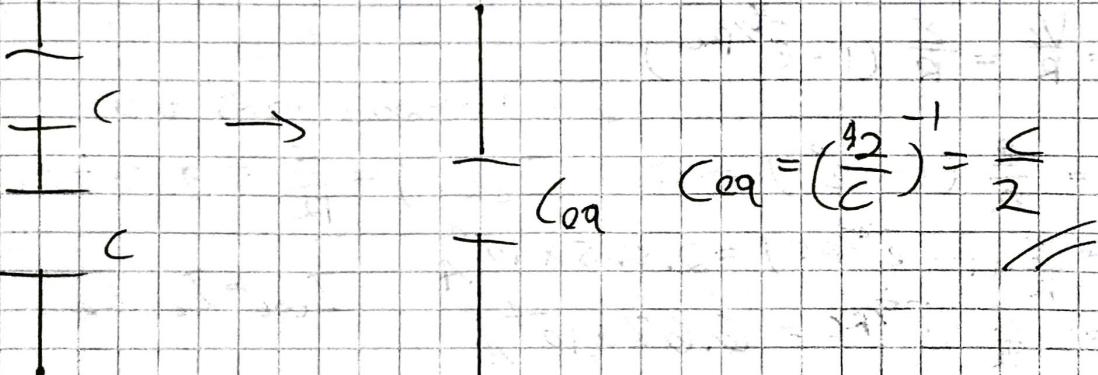
$$\frac{1}{C} + \frac{1}{T_c} \rightarrow \frac{1}{C_{eq}}, \quad C_{eq} = \frac{1}{\frac{1}{C} + \frac{1}{T_c}}$$



$$\frac{1}{C} + \frac{1}{T} \rightarrow \frac{1}{C_{eq}}, \quad C_{eq} = \left(\frac{1}{C} + \frac{1}{T}\right)^{-1}$$

```
[27] # Author Nadav Porat
import numpy as np
import matplotlib.pyplot as plt

emf = 30 # This is Epsilon, the battary.
R1 = 3000
R2 = 6000
C = 0.002
C *= 2
tau1 = (R1*C)
tau2 = (R2*C)
```

```
[30]
test = lambda t: emf*(-1*np.expm1(-t/tau1)) # expm1(x) is a function that returns [e^x -1]
v0 = test(20) # Setting the intial charge for discharge function.
voltage_fun = lambda t: emf*(-1*np.expm1(-t/tau1)) if t<20 else v0*np.exp(-t/tau2) # This function returns the voltage for 0<t<70
current_fun = lambda t: (emf/R1)*np.exp(-t/tau1) if t<20 else (v0/R2)*np.exp(-t/tau2)

time = np.linspace(0,70,140)
voltage = np.array(list(map(voltage_fun,time))) # Applying the functions to the Time domain.
current = np.array(list(map(current_fun,time)))
```



```
plt.figure() # Creating graphs

plt.subplot(211)
plt.title("V(t) and I(t) for 2C")
plt.ylabel("Current[A]")
plt.grid(True)
plt.plot(time,current,color="m")

plt.subplot(212)
plt.ylabel("Voltage [v]")
plt.xlabel("Time [sec]")
plt.grid(True)
plt.plot(time,voltage)
```